

1. Logic Gates

Logic Gates

- Logic gates are used to create the circuits that are used to perform computations in a computer.
- Different types of gates (below is only a subset):
 - NAND ("not AND")
 - AND
 - OR
 - NOR ("not OR")
 - XOR ("exclusive OR")