

4. Computation

Adding with logic gates: Half adder

Outputs: Sum and Carry

