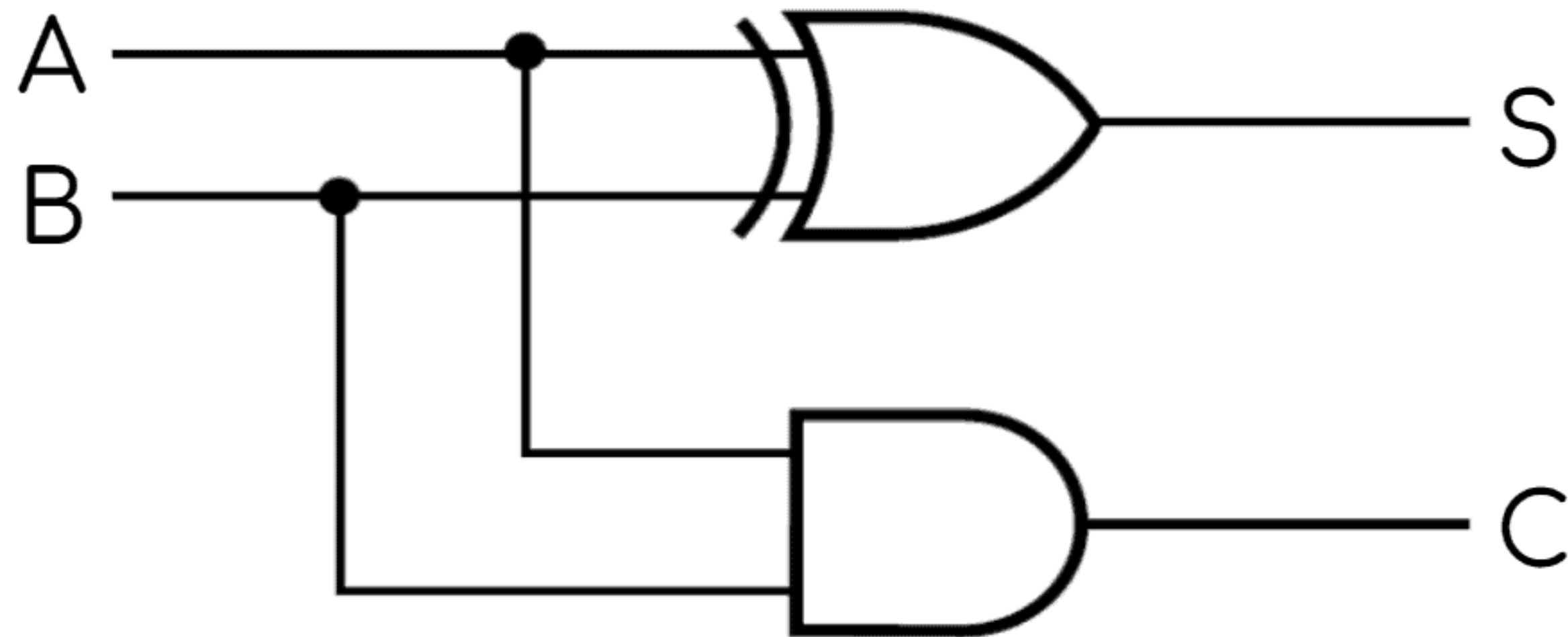


Adding with logic gates: Half adder

Outputs: Sum and Carry



Adding with logic gates: Full adder

Take a Carry bit as an input, in addition to the previous two inputs

