

Recap: Logic gates and transistors

- Transistors use complicated chemical interactions to behave like switches
- We can use these switches to create NAND gates
- We can use NAND gates to create all other types of logic gates

Next: using logic gates to store values

3. Memory