

AND and OR gates (cont.)

- Can visualize AND and OR gates with circuit diagrams
- Special symbols for common logic gates



AND gate



OR gate

NAND gate

- NAND gates are the basis for all circuits (not always, but we can assume it for now)
- We can use NAND gates to build every other type of logic gate
- NAND meaning: "not AND"



NAND gate

P	Q	P nand Q
TRUE	TRUE	FALSE
TRUE	FALSE	TRUE
FALSE	TRUE	TRUE
FALSE	FALSE	TRUE